
Experiment #4 – Integrated System

Moein Karami, 810198540

 $\begin{array}{c} \text{I. Frequency Multiplier} \\ f_{in} * 2^n = f_{ref} \; / \; k \; \Rightarrow 1 \; / \; T_{in} * 2^n \; = 1 \; / \; (T_{ref} \; * \; k) \; \Rightarrow \end{array}$

$$k = T_{in} / \left(\right. T_{ref} \, * 2^n)$$

A. State Diagram of the Controller:

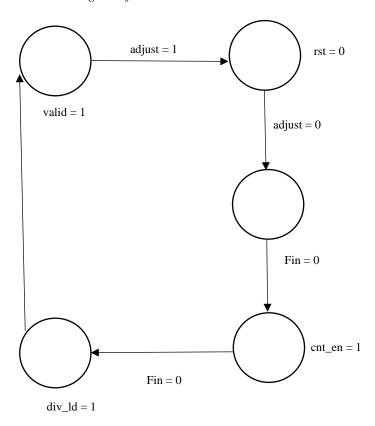

B. Simulate results: In all of wave forms InFreq = 1MHz Look at figures 1, 2 and 3.

II. EXPONENTIAL ACCELERATOR

A. Exponential Engine:

1) As you can see in figure 4 if we set

 \Diamond x = 0: answer will be 1


 \Diamond x = 1: answer will be e ~ 2.718

 \Diamond x = 0.5: answer will be $e^{0.5} \sim 1.648$

2) As you can see in figure 4 maximum frequency of this accelerator is equal to 135.01MHz.

B. Exponential Accelerator Wrapper:

1) Exponential Accelerator Wrapper Controller State diagram:

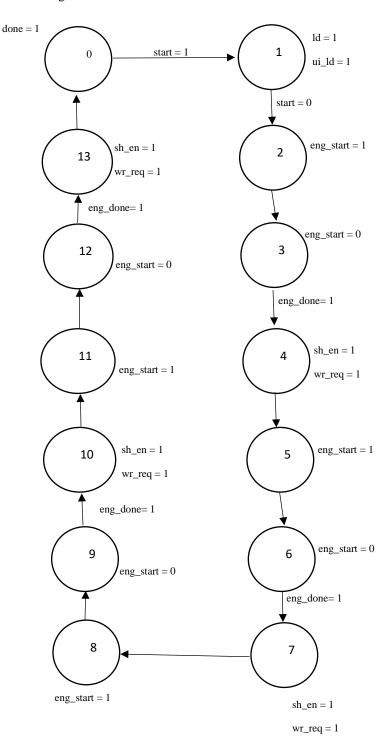

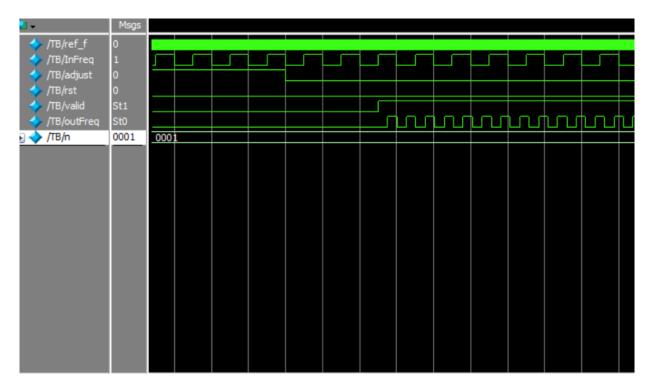


Fig. 1 n=1, outFreq frequency = 2MHz

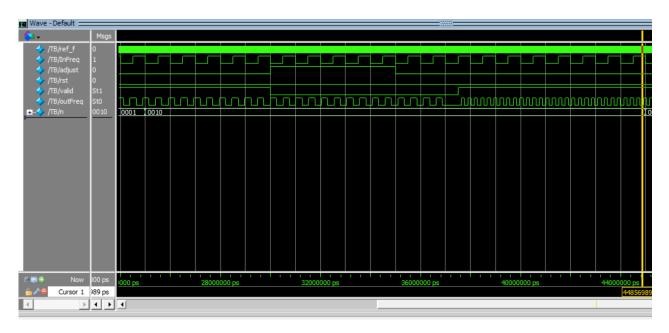


Fig. 2 n = 2, outFreq frequency = 4MHz

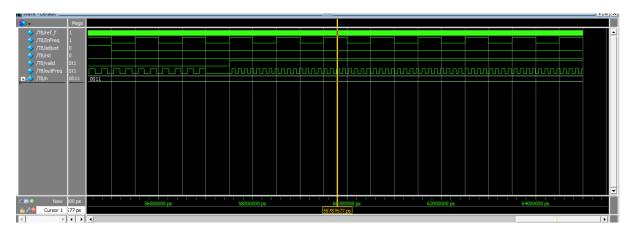


Fig. 3 n = 4, outFreq frequency = 8MHz

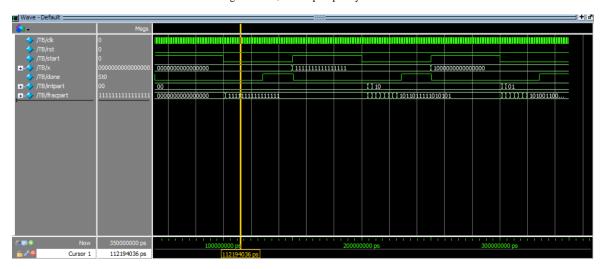


Fig. 4 simulate accelerator waveform

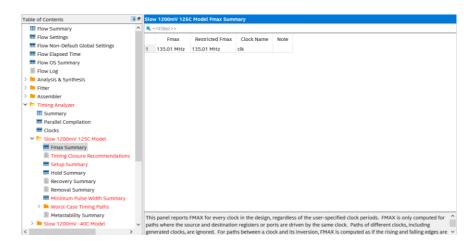


Fig. 5 Accelerator maximum frequency



Fig. 6 Wrapper maximum frequency

2) According to figure 6 its maximum frequency = 132.22MH

III. INTEGRATED CIRCUIT

1) MultFactor \leq 661 \rightarrow n \leq 5